

Electrical Network Analysis

Final Exam

Date: June 6th, 2026

Course Instructor(s)

Ms. Sara Kiran

Total Time: 3 Hours

Total Marks: 100

Total Questions: 05

Student Name

Roll No

Section

Student Signature

Do not write below this line


- Attempt all the questions. Round off answers to 2 decimal places.
- Attempt all parts of the same question together.
- Show all the steps with properly labelled circuit diagrams, direct answers are not acceptable.
- Attempt each question only ONCE

CLO #1: Apply circuit analysis techniques to determine the natural and forced response of second order circuits


Q.1

[4+16=20 marks]

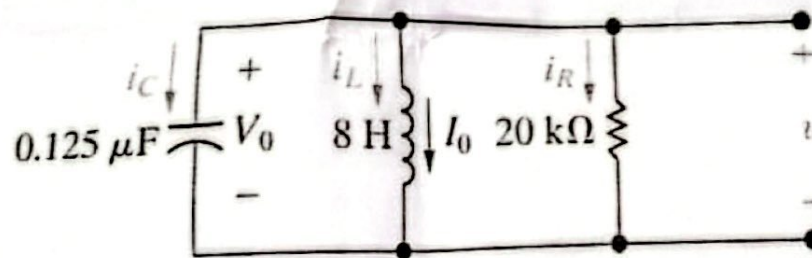- a. For the parallel RLC circuit shown below, **compute** the roots of the characteristic equation and **determine** the type of response for this circuit.



- b. For the Figure Shown below:

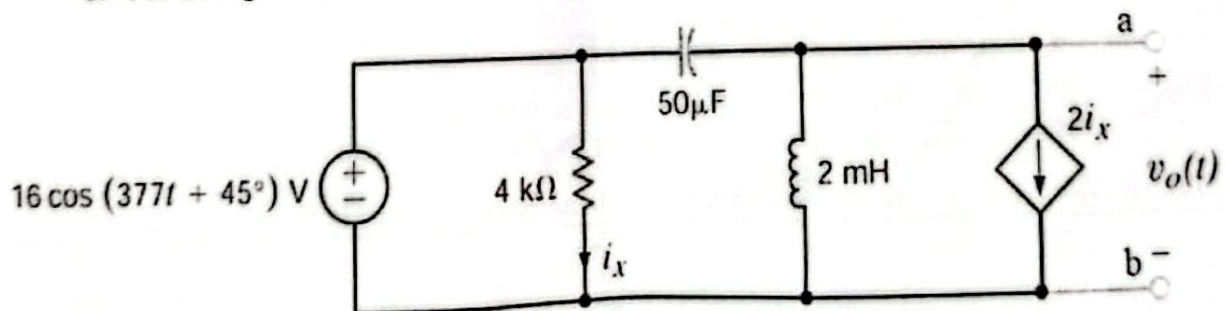


- Construct the frequency-domain equivalent circuit
- Apply node voltage method to compute the Thévenin voltage with respect to the terminals a and b
- Compute the Thévenin equivalent impedance
- Draw the Thévenin equivalent circuit

CLO # 2: Construct power triangle to compute power in AC circuits.

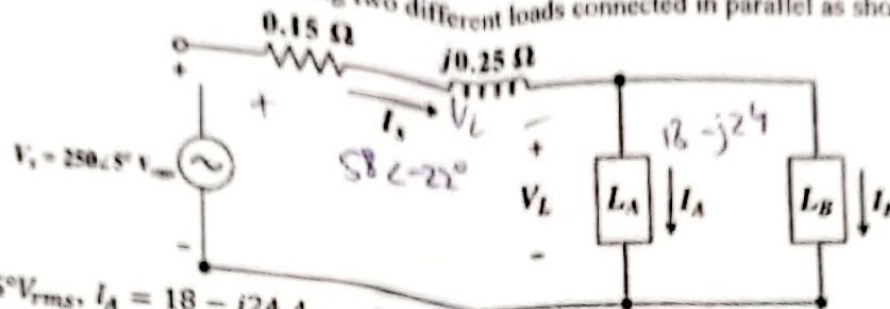Q.2

An alternating power supply V_s is feeding two different loads connected in parallel as shown below. [3+6+2+3+6=20 marks]



$V_s = 250 \angle 5^\circ V_{rms}$, $I_A = 18 - j24 A_{rms}$, $I_B = 58 \angle -22^\circ A_{rms}$. The transmission line impedance is $Z_{line} = 0.15 + j0.25 \Omega$.

- Compute the following:
 - I_s and V_L
 - Complex power absorbed by each load and the complex power delivered by the source
 - Overall power factor of the combined load
 - Power loss in the transmission line
- Construct power triangles for L_A and combined load

CLO # 3: Analyze balanced three-phase circuits to calculate electrical quantities.

Q.3

A balanced, three-phase circuit is characterized as follows:

[4+4+4+4+4 = 20 marks]

- Y- Δ connected;
 - Source voltage in the b-phase is $150 \angle 135^\circ$
 - Source phase sequence is abc
 - Line impedance is $2 + 3j \Omega$ per phase
 - Load impedance is $129 + 171j \Omega$ per phase
- Construct the single phase equivalent circuit for the a-phase
 - Calculate:
 - line currents; I_{aA} , I_{bB} and I_{cC}
 - per phase impedance of load 2
 - line voltages at the load end (V_{AB} , V_{BC} and V_{CA})
 - total complex power delivered to the Δ -connected load


CLO #4: Apply Laplace transform to determine the natural and forced response of RLC circuits.

Q4:

[10+7+3 = 20 marks]

Assuming zero initial conditions in the circuit given below:

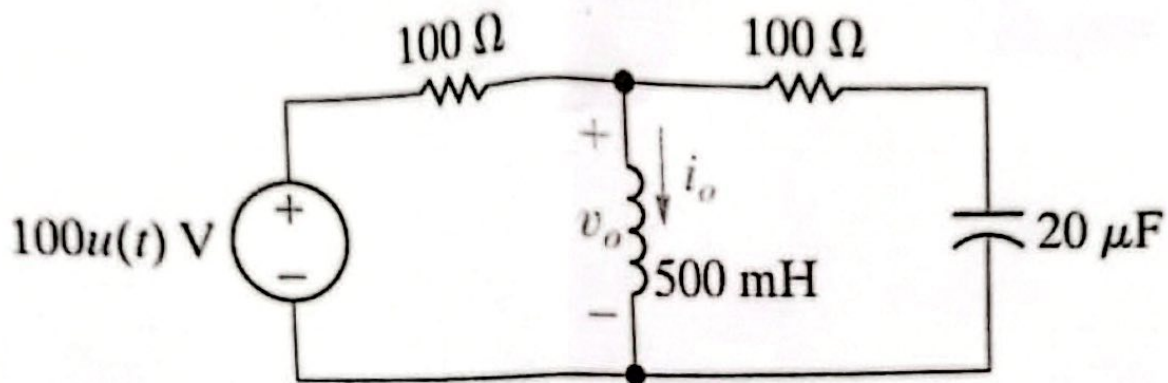- Transform the circuit in s-domain and determine the expression for voltage $V_o(s)$
- Compute $v_o(t)$ for $t \geq 0$
- Compute the value of $v_o(t)$ at $t = \infty$ using the final-value theorem




CLO #5: Analyze various types of filters using s -domain analytics.

Q5:

[4+4+4+4=20 marks]

For the given filter circuit:

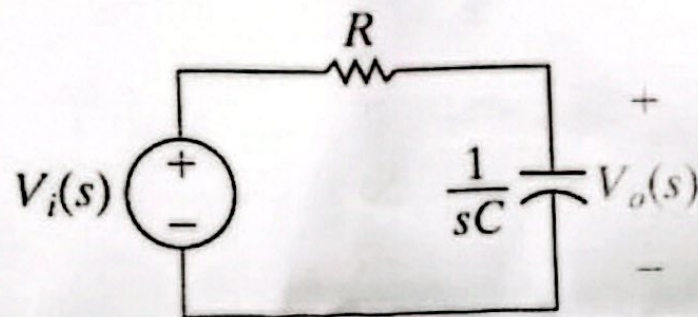

- Perform qualitative analysis to identify the type of filter.
- Determine the expression of the magnitude and phase of the transfer function $H(s)$ for the given filter circuit and sketch the magnitude plot.
- Calculate the cutoff frequency, and the magnitude of the filter's transfer function at ω_c , $0.5\omega_c$, and $2\omega_c$.
- Calculate value for R that will yield a low-pass filter with a cutoff frequency of 4 kHz ($C = 1\ \mu\text{F}$).