

Digital Logic Design
(EE1005)

Date: 21st February, 2026

Course Instructor(s)

Dr. Muhammad Naeem

Ms. Tamania Javaid

Sessional-I Exam

Total Time (Hrs): 1
Total Marks: 45
Total Questions: 3

Roll No

Section

Student Signature

Instructions:

- Attempt all the questions.
- Show complete working of each question.
- Multiple solutions of the same question will carry zero credit.
- State your valid assumptions clearly if you have to take any.

CLO #1: Describe various number systems and perform arithmetic operations and base conversions
[15 marks]

Q1:

Convert the following numbers from the given base to the other three bases listed in the table.
Show complete working on the answer sheet.

Decimal	Binary	Octal	Hexadecimal
69.3125	?	?	?
?	11101.0011	?	?
?	?	56.74	?
?	?	?	3B.02A

CLO #2: Apply Boolean algebra and K-map methods to optimize logic circuits

[15 marks]

Q2:

Consider the following Boolean expression

$$F(A, B, C, D) = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D})(A + B + \bar{D})(A + \bar{B} + C + D)$$

- ✓
- Apply the K-map method to find the optimized Boolean expression of the system in POS (product of sum) form.
 - Construct the logic circuit from the simplified expression using 2 input NAND gates only.


$$(B + \bar{D})(\bar{A} + \bar{B})(\bar{B} + C + D)$$

CLO #2: Apply Boolean algebra and K-map methods to optimize logic circuits

[15 marks]

Q3:

Consider the following digital circuit

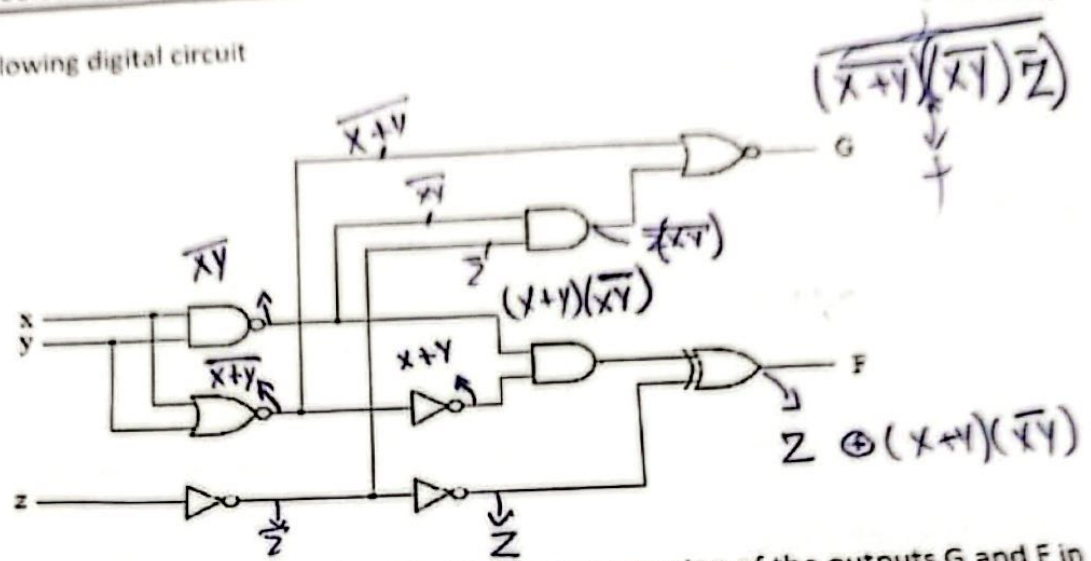

Construct the truth table and obtain the simplified Boolean expression of the outputs G and F in terms of inputs X, Y and Z.

NAND

MUL

NOR

Z

XOR

$(\overline{A}B + A\overline{B})$
 $(A \oplus B)$

