

	Course Name:	Linear Circuit Analysis	Course Code:	EE1001
	Program:	BS(Electrical Engineering)	Semester:	Spring 2023
	Duration:	60 minutes	Total Marks:	30
	Paper Date:	28-February-2023	Weightage:	15%
	Section:	All	Page(s):	2
	Exam Type:	MID - I		

- Instruction/Notes:
1. Circuits must be labeled properly, methods/techniques must be indicated and formulas must be written prior to inserting values.
 2. Show all steps.
 3. Attempt all parts of a question together.

Q.1

[10 marks]

[CLO 01]

The current $i(t)$ passing through a 10 mH inductor is given by the waveform shown in Figure 1 below:

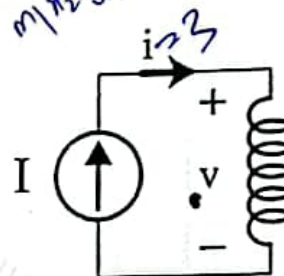
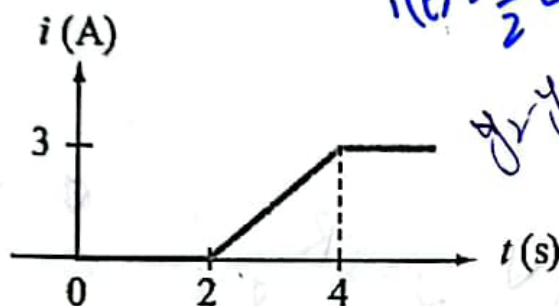


Figure 1. Waveform and Circuit for the current through the inductor

- Determine the piece-wise equation of the current from the graph.
- Determine corresponding voltage across the inductor and plot it.

Q.2 For the circuit shown in Figure 2 below: [10 marks]

[CLO 02]

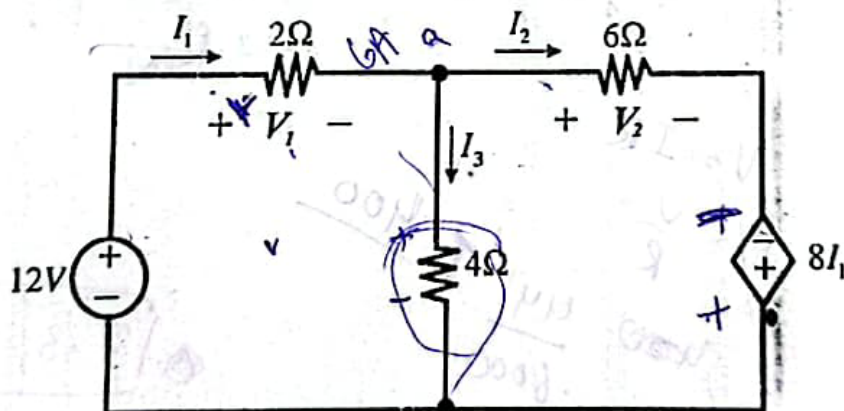
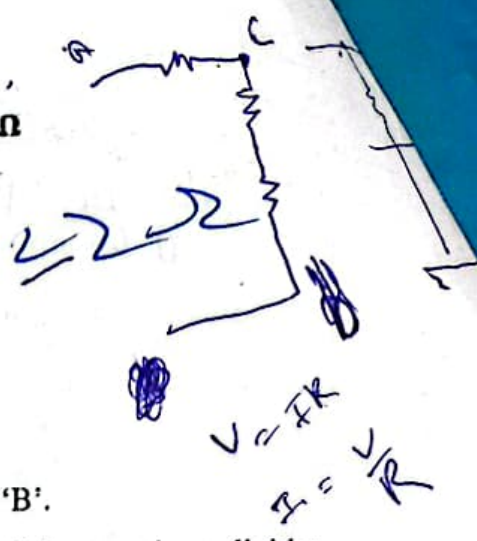


Figure 2. Circuit with Dependent Source

- Determine the voltages V_1 , V_2 and currents I_1 , I_2 using Kirchhoff's laws and Ohm's Law.
- Determine the power associated with the dependent voltage source using passive sign convention.

1CLO 0247


$$V = IR$$

$$I = \frac{V}{R}$$

- $$\begin{aligned} &= I R_1 + I R_2 + I R_3 \\ &= I V_1 + I V_2 + I V_3 \\ &= I (V_1 + V_2 + V_3) \end{aligned}$$

$$V = R_{\text{eq}} \times i_T$$

$$7.3 \times 10^{-3} \checkmark$$

$$I = \frac{V}{R}$$

④. 7.3 mV