



Power Electronics (EE3032)

Sessional-I Exam

Date: February 24, 2025

Course Instructor(s)

Dr. Muhammad Naeem

Total Time (Hrs): 1

Total Marks: 25

Total Questions: 3

Roll No

Section


Student Signature

Do not write below this line

Attempt all the questions.

CLO 1: Analyze op-amp application in power circuits.

Q1: Analyze the following high voltage, high current power amplifier circuit and calculate all the indicated dc voltages and currents. Ignore ac voltages and currents during analysis. [10]

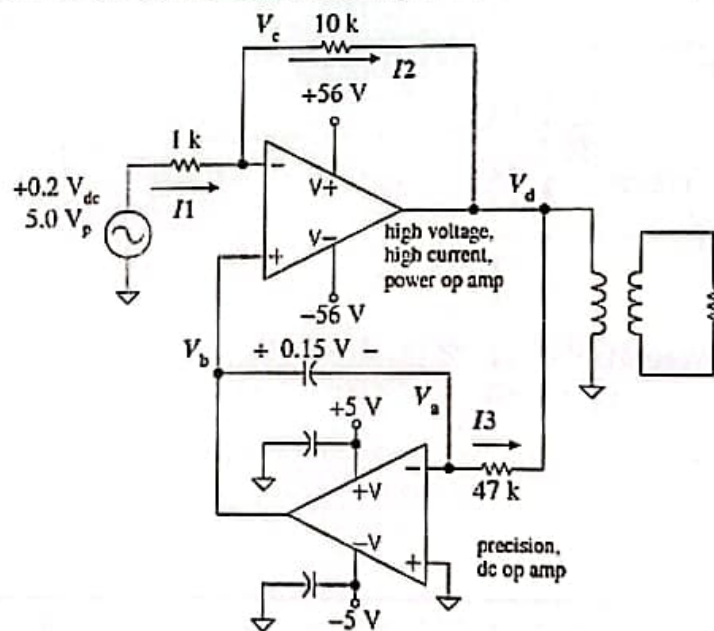

CLO 1: Analyze op-amp application in power circuits.

Q2: Analyze an op-amp circuit delivering a sine wave of $10 V_p$ to the 10Ω resistive load. The circuit is running from $\pm 24 V$ dc. Calculate the power delivered to the load, the power provided by the supply, and the power dissipated in op-amp in this circuit. [5]

✖

National University of Computer and Emerging Sciences
Lahore Campus

CLO 2: Analyze audio power amplifier circuits.

Q3: In the following audio amplifier circuit, an audio signal is applied at non-inverting input terminal and the output is delivered to an $8\ \Omega$ speaker. Analyze the working of this circuit and calculate all the indicated voltages (both dc and rms values). Also analyze how much dc and ac power is delivered to the speaker. [10]

